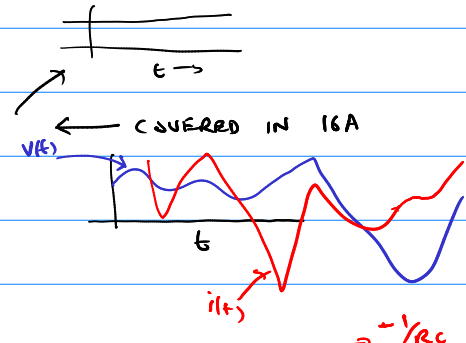


→ RECAP

→ 3 DIFFERENT TYPES OF CIRCUIT ANALYSIS

→ DC: all voltages/currents unchanging w time

→ SIMPLE ALGEBRAIC EQNS: $i = \frac{V}{R}$, $V_2 = \frac{R_2}{R_1 + R_2} V_1$




→ transient: " " CHANGING WITH TIME

→ DIFFERENTIAL EQNS: $i(t) = C \frac{dv}{dt}$, $C \frac{dv(t)}{dt} = -\frac{v(t)}{R}$ (or $\frac{dv}{dt} = -\lambda v(t)$)

→ SOLUTION $v(t) = V_0 e^{-\lambda t}$
→ ALL YOU NEED TO KNOW ODES → INITIAL CONDITION: $V_0 = v(0)$

KRIS: SHOWED THIS SOLVES ODE ← HW: SHOWS ONLY THIS SOLVES IT

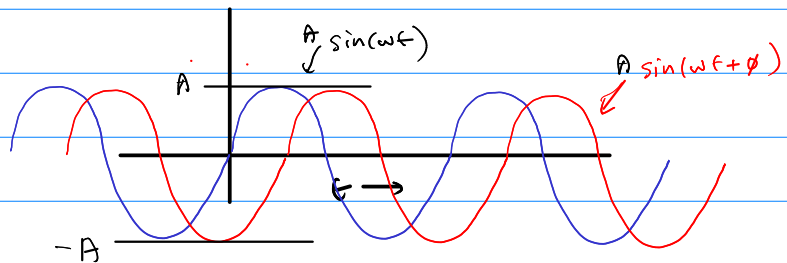→ SPECIAL CASE: everything changing SINUSOIDALLY with time



→ SPECIAL TYPE OF CONVENIENT ANALYSIS: SINUSOIDAL S. STATE

→ PHASORS

→ FREQ. DOMAIN TRANSFER FUNCTIONS

→ ALL SOLVING THE SAME CRT / PROBLEM
→ IN DIFFERENT WAYS


→ TRANSIENT: MOST GENERAL (BUT MOST INVOLVED)

→ DC: EASY AND IMPORTANT (BUT LIMITED USES)

→ SINUSOIDAL STEADY-STATE: ALMOST-TRANSIENT (BUT EASIER AND MORE INSIGHTFUL THAN TRANSIENT)

→ WHY ARE SINUSOIDS IMPORTANT / INTERESTING

→ DEMO

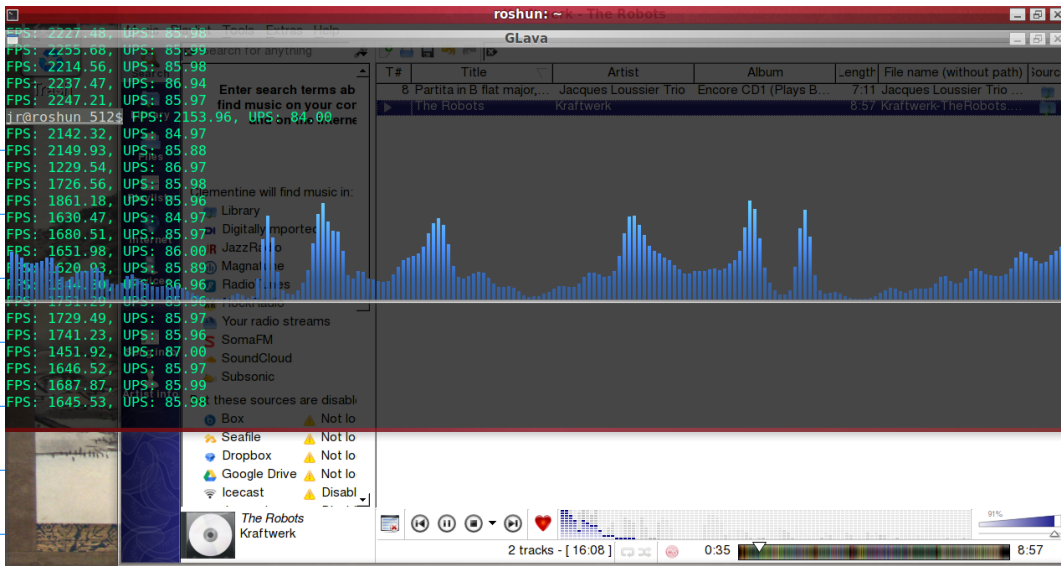


→ VOICE / MUSIC etc CAN BE REPRESENTED AS A SUM OF MANY SINUSOIDS (AT DIFFERENT FREQS.)

→ CHANGING THE RELATIVE STRENGTHS OF DIFFERENT SINUSOIDS: FILTERING


→ SINUSOIDAL ANALYSIS: STEP TOWARDS UNDERSTANDING THIS.

→ LATER: DFT ; LATER: EE120

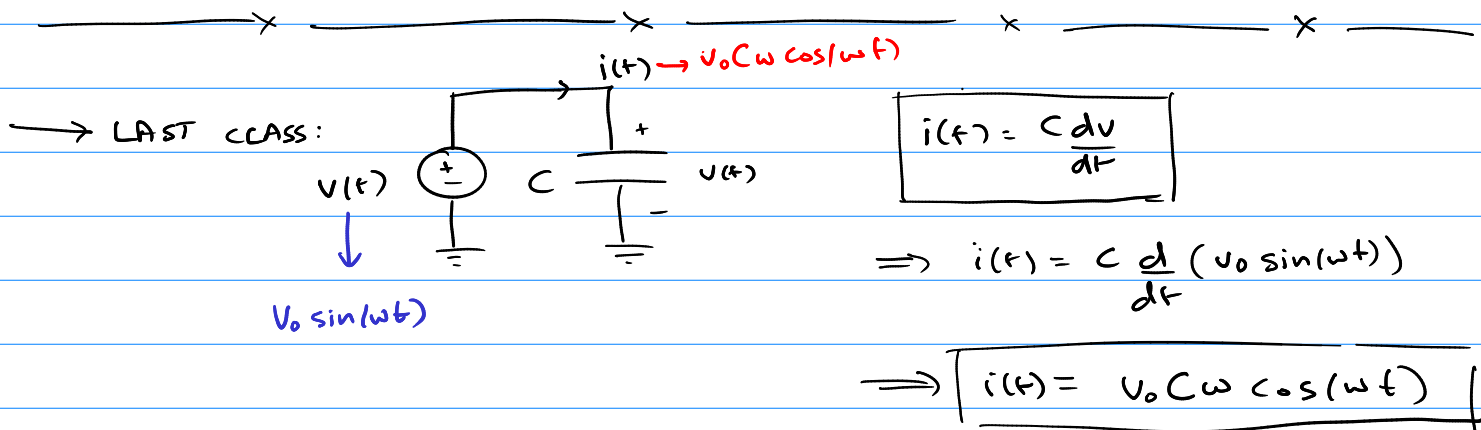

→ COMPARE w RESISTOR

$$i(t) = \frac{v(t)}{R}$$

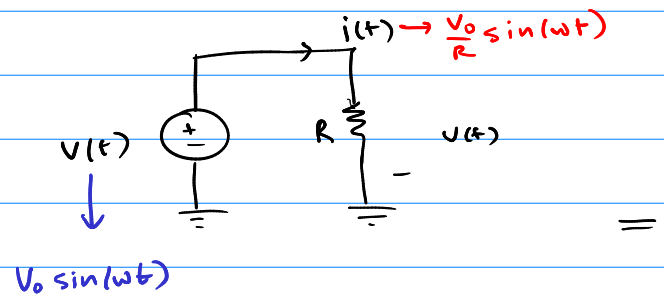

$$\Rightarrow R = \frac{v(t)}{i(t)}$$

CHECK:

$$\frac{V_0 \sin(\omega t)}{\frac{V_0}{R} \sin(\omega t)} = R \quad \checkmark$$

→ WHAT IS $\frac{v(t)}{i(t)}$ FOR A CAP. WITH SIN. INPUT?

CAP: $\frac{v(t)}{i(t)} = \frac{\cancel{v_0 \sin(\omega t)}}{\cancel{v_0 C \omega \cos(\omega t)}} = \frac{1}{C\omega} \sin(\omega t) \leftarrow ???$

↑
depends on input freq?

↳ "resistance" depends on time?
↳ goes to ∞ ?
↳ becomes -ve?

→ SEEMS TO COMPLICATED COMPARED TO RES.

→ CAN WE DO BETTER?

————— x ————— x ————— x —————

→ THE KEY (as it turns out): express $\sin()$ / $\cos()$ USING
COMPLEX NUMBERS

→ RESOURCES: → TUTORIAL by TAs (up last night)

→ short recap: this week's discussion.

→ very short RECAP:

→ $j = \sqrt{-1}$: imaginary number $\Rightarrow j^2 = -1$

→ $a = a_r + j a_i$: complex number

↑ ↑
real part imag. part

→ follows usual rules of addition/mult./etc:

$$\begin{aligned} \rightarrow c = a \pm b &= (a_r + j a_i) \pm (b_r + j b_i) \\ &= \underbrace{(a_r \pm b_r)}_{c_r} + j \underbrace{(a_i \pm b_i)}_{c_i} \end{aligned}$$

→ CONJUGATE of complex numbers:

Given $a = a_r + j a_i$

→ $\overline{a} \triangleq a_r - j a_i$ (change sign of imag. part)

conjugate
(unrelated
to logical NOT)

→ $a + \bar{a} = \text{ALWAYS REAL!}$ ← V. IMP.

$$\rightarrow (a_r + j a_i) + (a_r - j a_i) = \frac{2a_r}{\uparrow \text{real}}$$

→ $a - \bar{a} = \text{ALWAYS IMAG.} = 2j a_i$

EXTREMELY IMP.

→ RELATION TO $\sin()/\cos()$: de MOIVRE'S THM.

$$e^{j\theta} = \cos(\theta) + j \sin(\theta)$$

← "DMT"

→ USING DMT, can write $\sin()/\cos()$ using $e^{j\theta}$ & $e^{-j\theta}$:

$$\rightarrow e^{j\theta} = \cos(\theta) + j \sin(\theta)$$

$$+ e^{-j\theta} = \cos(\theta) - j \sin(\theta)$$

[using $\cos(-\theta) = \cos(\theta)$ & $\sin(-\theta) = -\sin(\theta)$]


$$e^{j\theta} + e^{-j\theta} = 2 \cos \theta$$

$$\Rightarrow \boxed{\cos(\theta) = \frac{e^{j\theta} + e^{-j\theta}}{2}}$$

→ SUBTRACT:

$$\boxed{\sin(\theta) = \frac{e^{j\theta} - e^{-j\theta}}{2j}}$$

WILL USE THESE

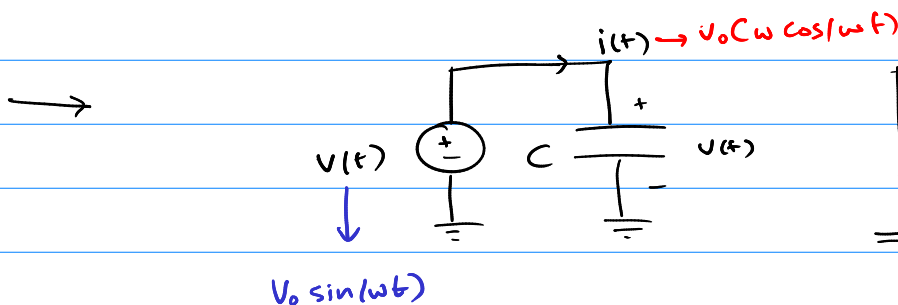

$$\boxed{i(t) = C \frac{dv}{dt}}$$

$$\Rightarrow i(t) = C \frac{d}{dt} (V_0 \sin(\omega t))$$

$$\rightarrow V_0 \sin(\omega t) = \frac{V_0}{2j} [e^{j\omega t} - e^{-j\omega t}] \Rightarrow i(t) = C \frac{d}{dt} [e^{j\omega t} - e^{-j\omega t}]$$

$$\Rightarrow i(t) = \frac{V_0}{2j} C j \omega [e^{j\omega t} + e^{-j\omega t}] = V_0 \omega C \times \frac{1}{2} [e^{j\omega t} + e^{-j\omega t}] \rightarrow \cos(\omega t)$$

→ FOR THE CAP W SIN. INPUT :

$$v(t) = \frac{V_0}{Z_j} e^{j\omega t} - \frac{V_0}{Z_j} e^{-j\omega t}$$

$$i(t) = \frac{V_0 C \omega}{2} e^{j\omega t} + \frac{V_0 C \omega}{2} e^{-j\omega t}$$

→ LOOK AT JUST THE COEFFS OF $e^{j\omega t}$

$$\tilde{V} = \frac{V_0}{Z_j}, \quad \tilde{I} = V_0 \frac{C\omega}{2}$$

PHASOR OF $v(t)$ PHASOR OF $i(t)$

PHASORS

$$v(t) = \tilde{V} e^{j\omega t} + \overline{\tilde{V}} e^{-j\omega t}$$

COMPLEX CONJUGATES

COMPLEX CONJUGATES

$$i(t) = \tilde{I} e^{j\omega t} + \overline{\tilde{I}} e^{-j\omega t}$$

COMPLEX CONJUGATES!

→ SO: THEY ALWAYS ADD TO REAL

→ $v(t)/i(t)$ ALWAYS REAL AND NEVER COMPLEX!
↑ NEVER!

→ BUT THEIR PHASORS ARE COMPLEX

→ WHY ARE PHASORS USEFUL / INTERESTING?

→ TRY

$$\frac{\tilde{V}}{\tilde{I}} = \frac{\frac{V_0}{Z_j}}{V_0 \frac{C\omega}{2}} = \frac{1}{j\omega C}$$

Like a resistance,
but depends on ω


angular
freq.

"IMPEDANCE"
OF CAPACITOR
↓ Z_C

→ RELATES v & i PHASORS

$$\tilde{I} = \frac{\tilde{V}}{Z_C}$$


→ YOU CAN ANALYSE CIRCUITS WITH PHASORS!

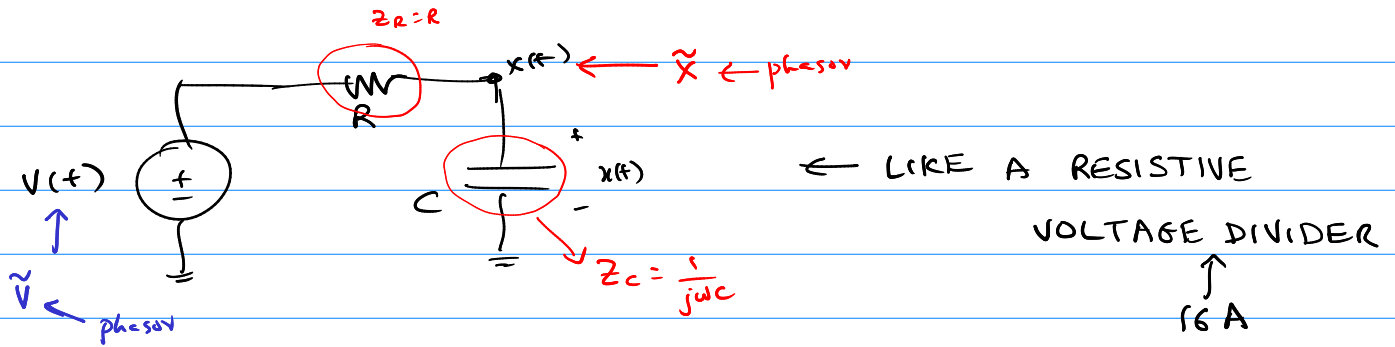



$$\tilde{X} = \tilde{V} \frac{Z_C}{R + Z_C} = \tilde{V} \left(\frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \right) = \tilde{V} \frac{1}{1 + j\omega RC}$$

$$\rightarrow \tilde{X} = \tilde{V} \times \frac{1}{1 + j\omega RC}$$

↑ ↑
voltage phasors.

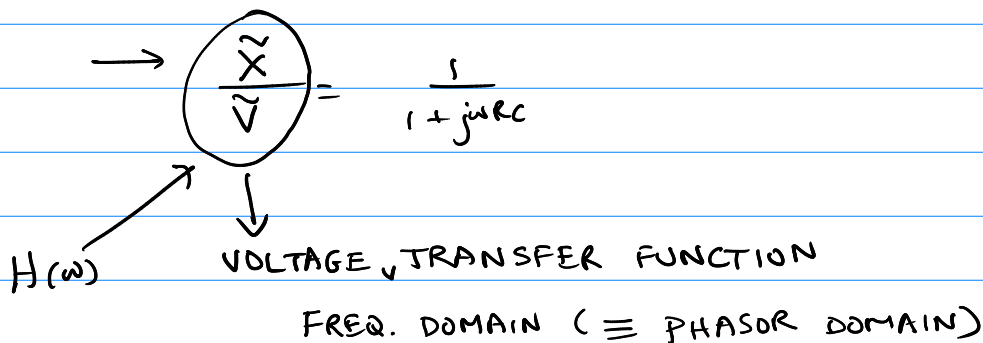

→ ENABLES A SYSTEM VIEW OF THE CRT.

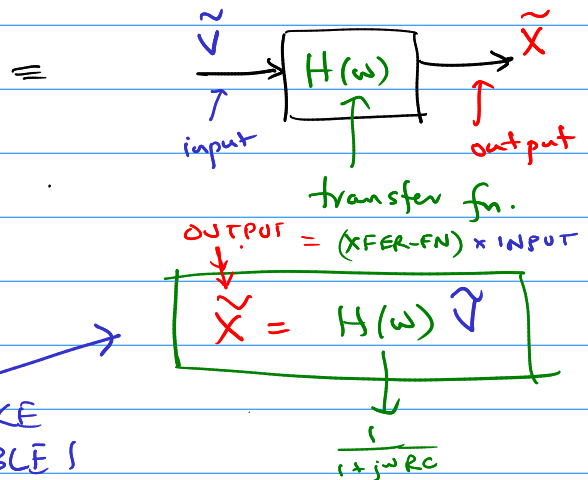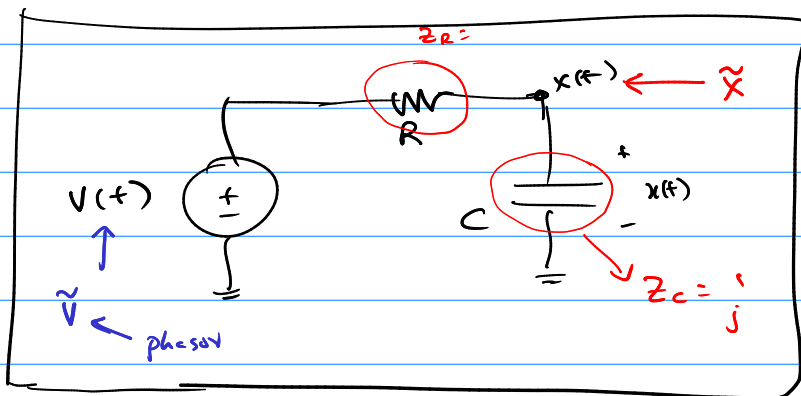

PHASORS MAKE THIS POSSIBLE!



→ WHAT HAVE WE ACHIEVED?

→ GIVEN SINUSOIDAL $v(t) = \tilde{V} e^{j\omega t} + \text{c.c. term}$
 phasor $\tilde{V}$ ← given this

→ FOUND $\tilde{X} = \text{phasor for } x(t) = \tilde{V} H(\omega) = \frac{\tilde{V}}{1+j\omega RC}$

→ Now, we can find $x(t)$ very easily.


→ $x(t) = \tilde{X} e^{j\omega t} + \text{c.c. term.}$
 $= \frac{\tilde{V}}{1+j\omega RC} e^{j\omega t} + \text{c.c. term}$
 express in polar form: $|\tilde{X}| e^{j\theta}$

→ DISCUSSION

$$|\tilde{X}(\omega)| = \frac{|\tilde{V}|}{\sqrt{1+\omega^2 R^2 C^2}}, \quad \theta(\omega) = \angle H(\omega) = -\tan^{-1}(\omega RC)$$


$$\Rightarrow x(t) = |\tilde{X}(\omega)| e^{j(\omega t + \theta)} + \text{c.c. term}$$

$$\Rightarrow \boxed{x(t) = 2 |\tilde{X}(\omega)| \cos(\omega t + \theta)}$$

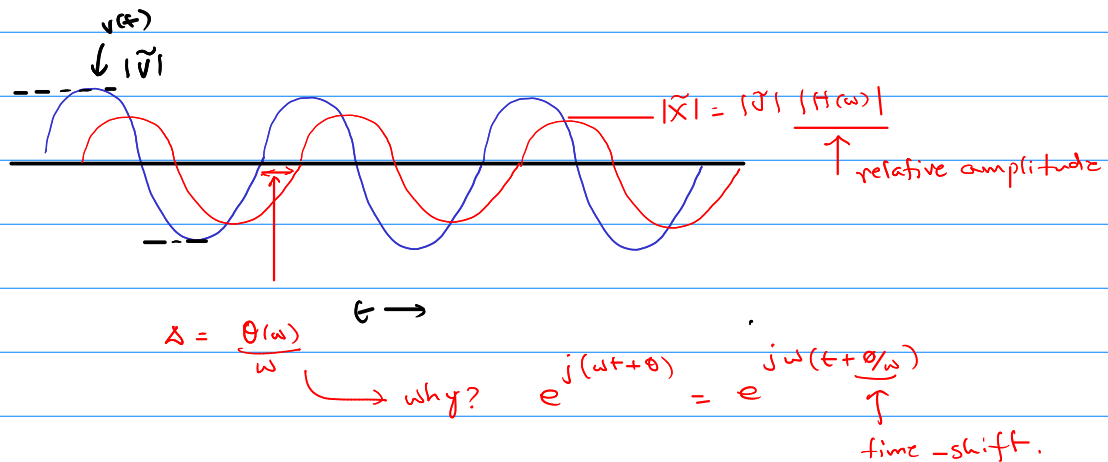

→ OSCILLOSCOPE DEMO (NUMERICAL)

→ OSCILLOSCOPE DEMO

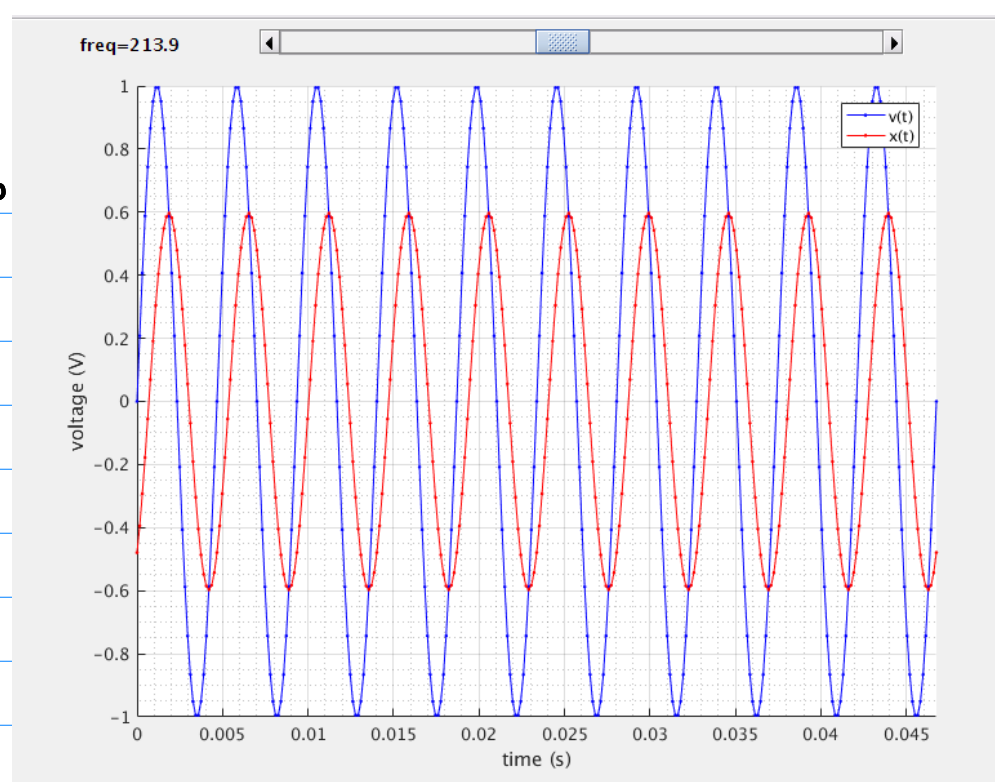

→ SUMMARY: WHAT HAVE WE DONE TODAY

→ DEMO (AUDIO): MANY SINUSOIDS AT DIFFERENT FREQS = VOICE / MUSIC / ETC.

→ SINUSOIDS CAN BE WRITTEN USING COMPLEX NUMBERS + C.C.

→ PHASOR: coeff. of $e^{j\omega t}$

→ IN "PHASOR DOMAIN": CAP LOOKS LIKE RESISTOR

↳ IMPEDANCE depends on ^{angular} freq ω

→ CIRCUITS CAN BE SOLVED IN PHASOR DOMAIN $= 2\pi f$

↳ BIG WIN OVER SOLVING DIFF. EQNS.

↳ BUT VALID ONLY IF ALL WAVEFORMS SINUSOIDAL.

→ IN PHASOR DOMAIN: RATIOS OF VOLTAGES / CURRENTS

ARE SIMPLE EXPRESSIONS IN ω (eg, $\frac{1}{1+j\omega RC}$)

→ TRANSFER FUNCTIONS $H(\omega)$: output = $H(\omega) \times$ input

↑
"FREQ. DOMAIN"

↑
PHASORS

→ CAN EASILY RECOVER TIME DOMAIN (eg $x(t)$, $i(t)$)

From PHASORS.